

# **CSE 260M / ESE 260**

# **Intro. To Digital Logic & Computer Design**

Bill Siever  
&  
Michael Hall

# Announcements

- Homework 1: Returned tomorrow
  - Can request “regrade” of problems for ~1 week on assignments  
Not accepted after that.
- Homework 3A Posted / Due Sunday at 11:59pm
  - Dropboxes posted Thursday
- Fee: \$65 will be applied to student accounts in coming week(s)

# Review

- Negation Notation
  - $\overline{AB}$  vs.  $\overline{A} \cdot \overline{B}$ 
    - $\overline{A} \cdot \overline{B} = \overline{AB}$
- K-Maps: What & why?
- Glitches

**Goal: Store Data**

# Examples


- Bistable Example 1: Inverters
- Bistable Example 2A: Inverters & some control
- Bistable Example 2B: Inverters, control, and ...

# Story Time: Latches

# Stable, Reinforcing Setup: SR Latch

- On-line Demo: <https://logic.ly/>
  - Bistable: Two stable configurations
- Goal: Met!
  - S=Set, R=Reset

# SR Latch

 




# Goal: Store Data

- Set/Reset is *inconvenient*
  - We want something like,  $\text{data} = X$ , where  $x$  is 0 or 1 (store  $X$ , not “set or reset data based on  $X$ ”)
  - We want to store  $X$  in data *when we're ready to!*
- *Clock (Clk)*: Indicates *when* we want to change the data

# D-Latch

- Start with SR Latch

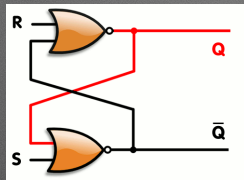


- Describe Desired Behavior (of output, Q)

CLOCK	DATA	Q
0	0	(Unchanged)
0	1	(Unchanged)
1	0	0
1	1	1

# D-Latch

- Start with SR Latch

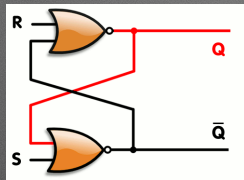


- Describe Desired Behavior (of output, Q)

CLOCK	DATA	Q
0	0	$Q_{prev}$
0	1	$Q_{prev}$
1	0	0
1	1	1

# D-Latch

- Start with SR Latch

 


- Describe Desired Behavior (of output, Q)

CLOCK	DATA	Q
0	0	$Q_{prev}$
0	1	$Q_{prev}$
1	0	RESET
1	1	SET

# D-Latch


- Start with SR Latch

 

- Describe Desired Behavior (of output, Q)
- Just combinational logic

CLOCK	DATA	Q
0	0	$Q_{prev}$
0	1	$Q_{prev}$
1	0	RESET
1	1	SET

# D-Latch

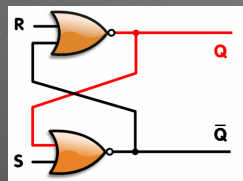


- Start with SR Latch
- Describe Desired Behavior (of output, Q)
- Just combinational logic
- Reset = Clock \* /Data  
Set = Clock \* Data

CLOCK	DATA	Q
0	0	$Q_{prev}$
0	1	$Q_{prev}$
1	0	RESET
1	1	SET

# Updates: D-Latch

# D-Latch

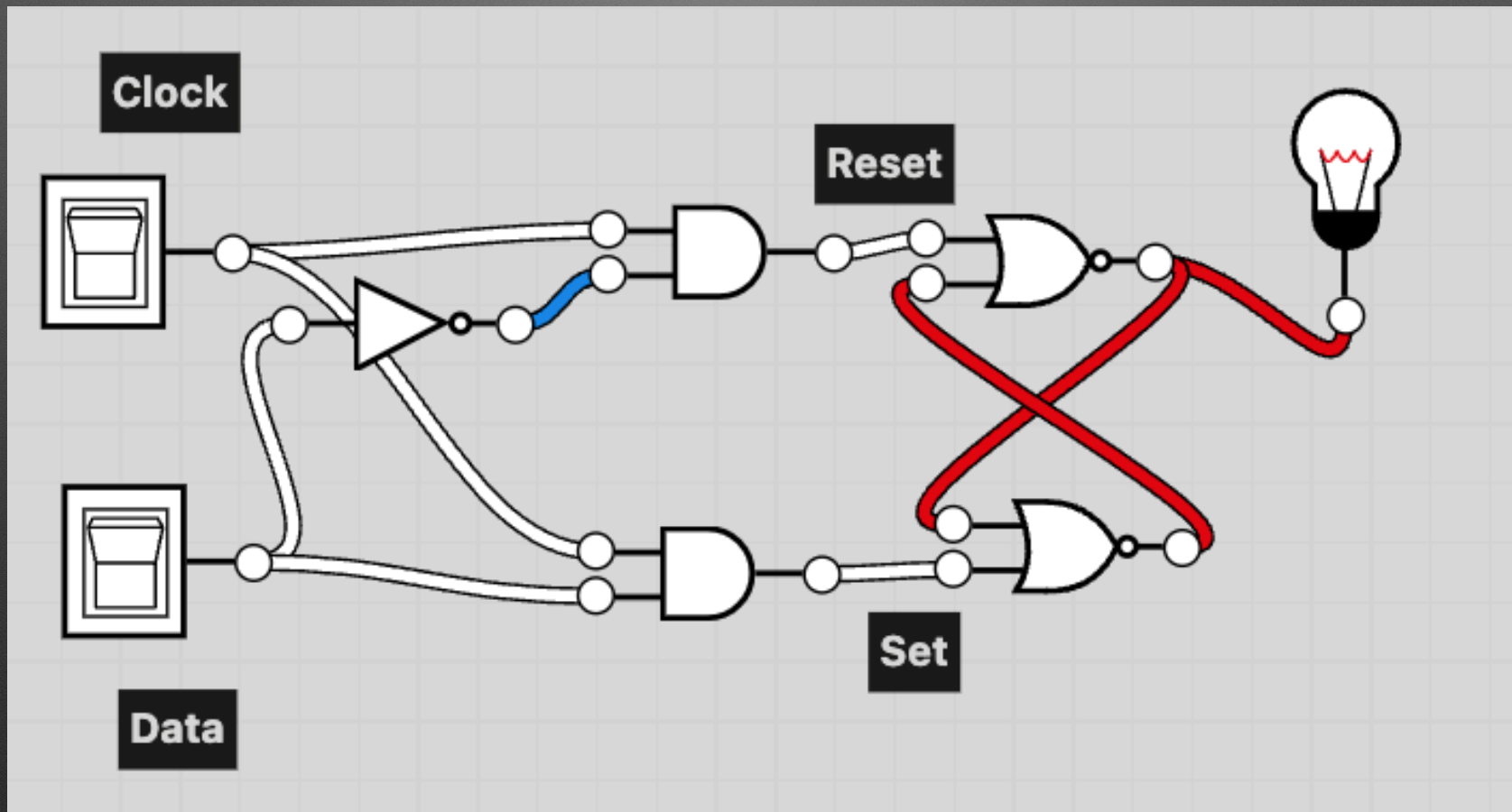



# D-Latch

- “Latches on” to last data value when clock goes low
  - Is sensitive to the level of the clock
  - Is “transparent” when the clock is high

# Goal: Store Data

- D-Latch is *still* a bit *inconvenient*
  - We'd like something like a (simple) camera
  - The instant shutter is “pressed” we capture data *at that exact instant* (no transparent phase)

# Flip-Flop




<https://openclipart.org/detail/288726/flip-flops-4>

# D Flip-Flop

- Two D-Latches with clocks in opposite states (via an inverter)
  - First stage: Transparent when clock is Low
  - Second stage: Transparent when clock is High
  - Effect: Capture D at precise instant clock goes from low to high
    - I.e. the clock EDGE
    - Edge triggered. Specifically, Rising Edge Triggered

# Signal Edges

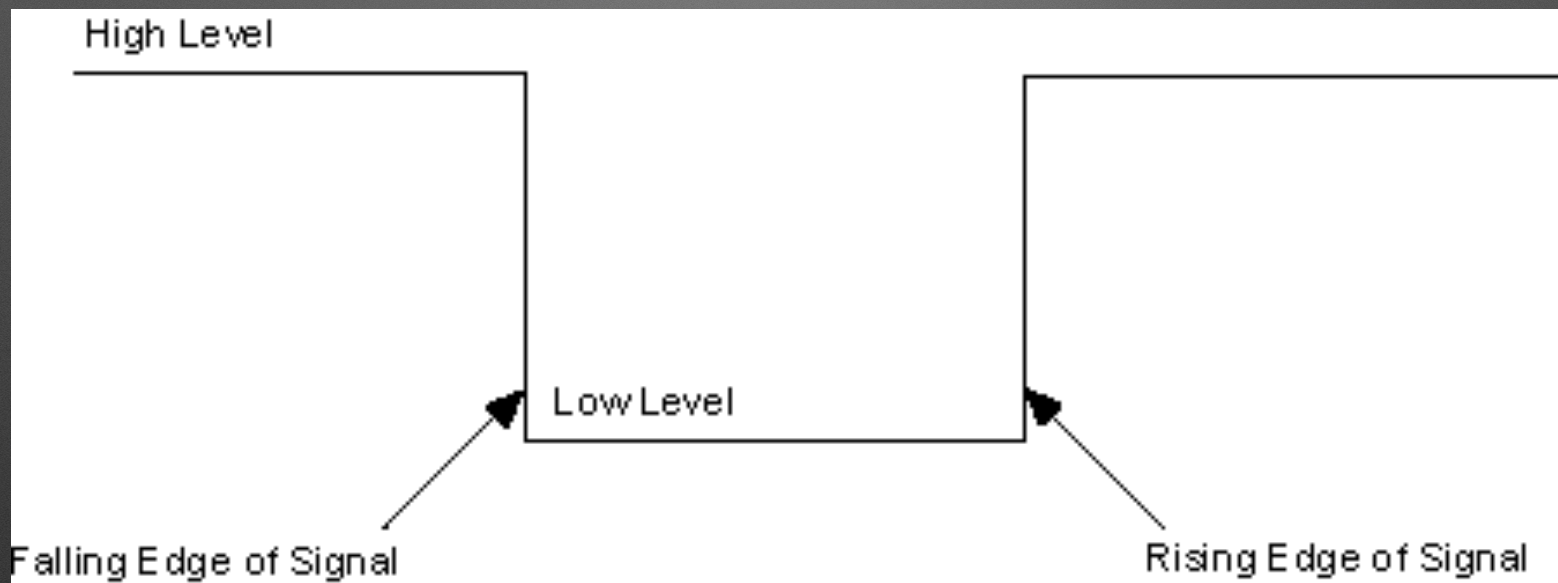


[https://www.ni.com/docs/en-US/bundle/ni-hsdio/page/hsdio/fedge\\_trigger.html](https://www.ni.com/docs/en-US/bundle/ni-hsdio/page/hsdio/fedge_trigger.html)

# Updates: D-Flip-Flop
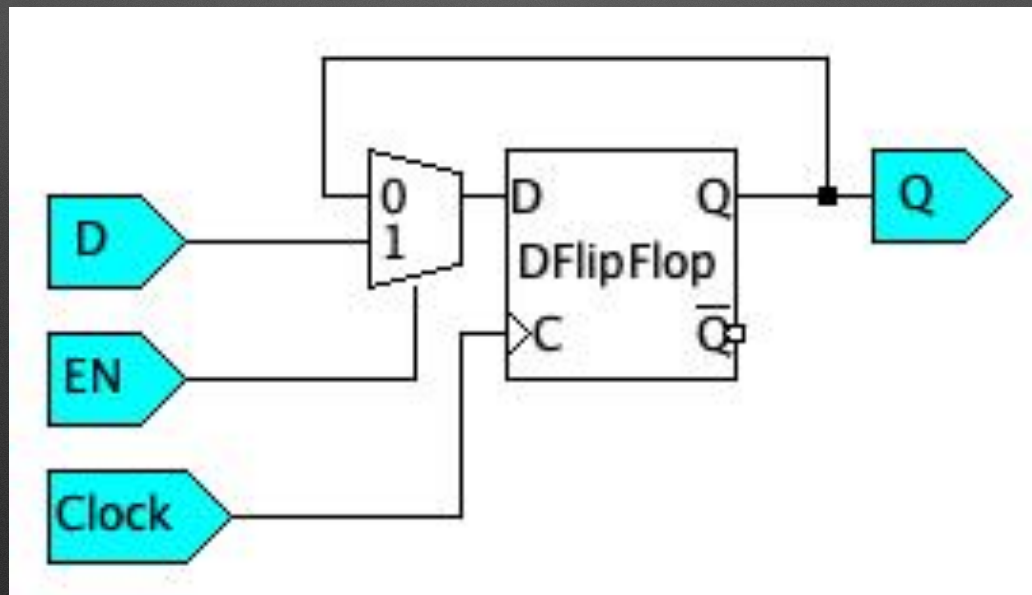
# “Enable”

- We may want to have two things control timing: the clock and an enable
- Ex:  $X[0] = 1$  (in a program) . We only want to modify  $X$  *when that line runs*.



# Chapters 1-2: Combinational Logic

- (Purely) combines current inputs to produce output
  - Doesn't depend on past inputs
  - Can be represented with a simple table
  - One-way: Doesn't have any feedback paths from output back to inputs





# Chapter 3: Sequential & Synchronous Logic

- Need to know sequence of inputs
  - Can't be represented with a *simple* table of just inputs and outputs (Possibly a complex table that includes some representation of history of inputs and outputs)
- Text: "Some sequential circuits are just plain kooky"

# Synchronous\* Sequential Circuits

- Are synchronized by a common clock
- Uses registers (D Flip Flops)
- Mix of registers and combinational logic
- Cycles in circuit include at least one register
- Goal: Impose predictable behavior!

\* eliminates the “kooky”


# Finite State Machines

- State: A condition of being
- Finite: Er. Finite
  - Real machine has real-world limitations:  $k \times$  D-latches
  - $k$  D-Latches means  $\leq 2^k$  states (finite)


# FSM Applications

- Things with modes or sequences of steps. Examples:
  - Washing Machine (fill, agitate, rinse, spin)
  - Stop lights & Traffic control: Green, Yellow, Red
  - Locks: Locked & unlocked
  - Computer programs: Playing game vs. on menu
  - Elevator controls (state = floor)
  - ...

# Book Example Variation: Stop Light

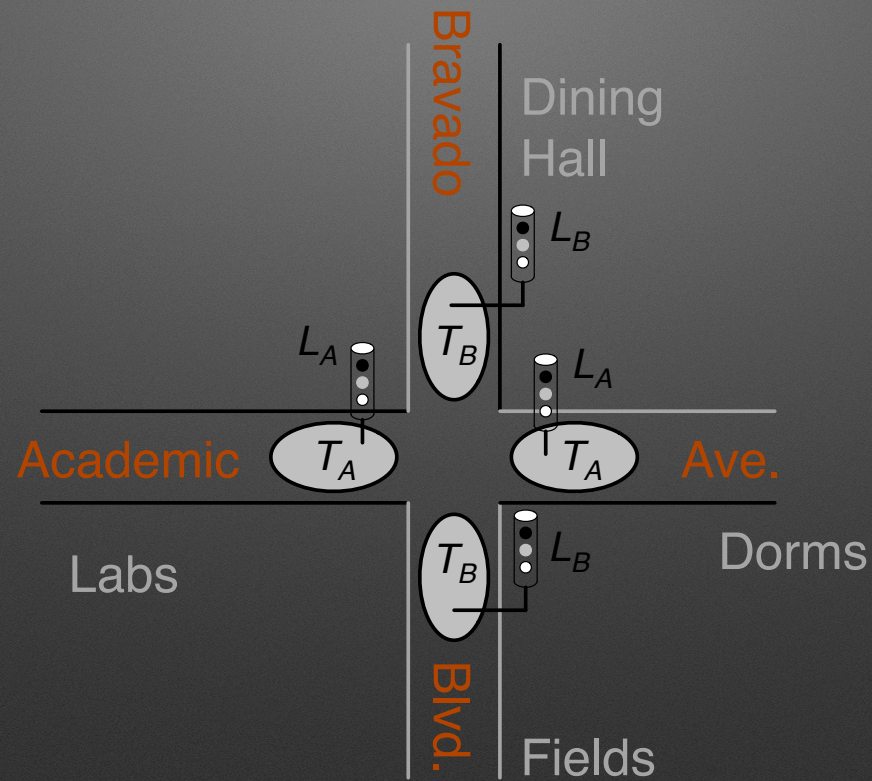


# FSM: Moore Machine Structure

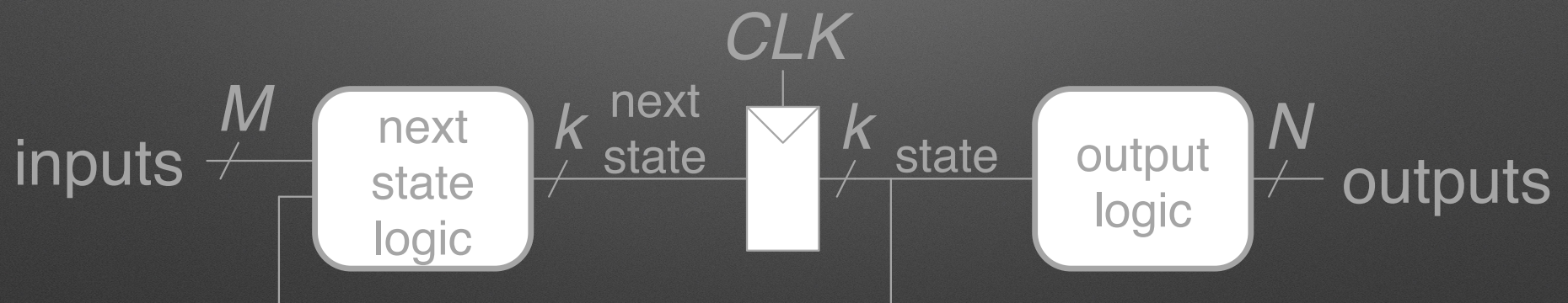

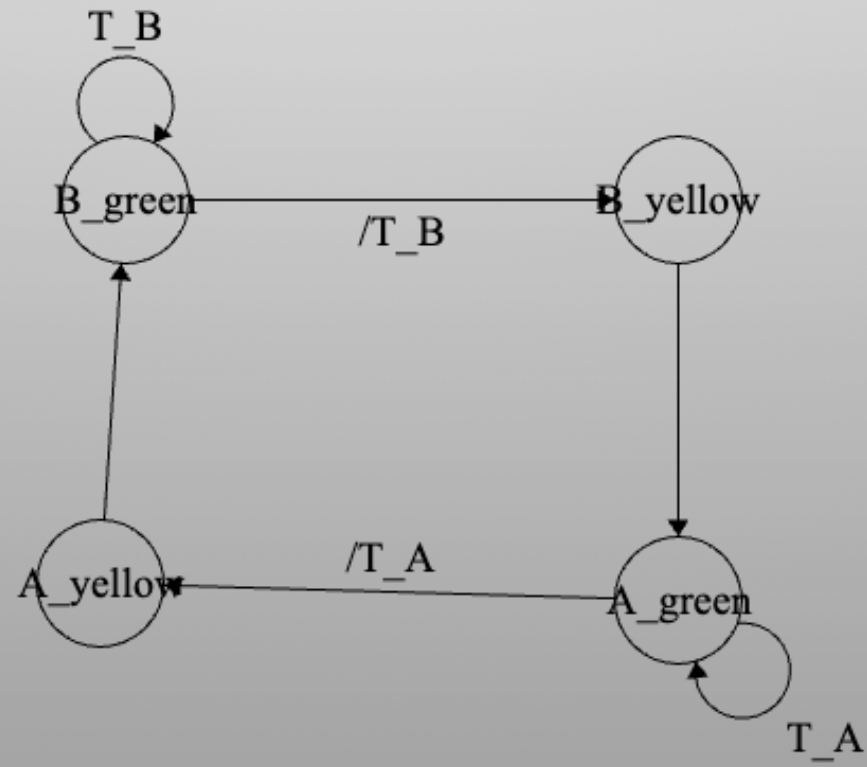
# Background

- Clock is 5s: minimum time in a state
- Need to describe behavior over time
- State diagram forms
  - FSM Designer: <https://wilsonem.github.io/fsm/>
- Example: Variation on textbook;  
Different output signals and “one hot” encoding






# FSM: Mealy Machine

 

# FSM: Moore Machine Structure

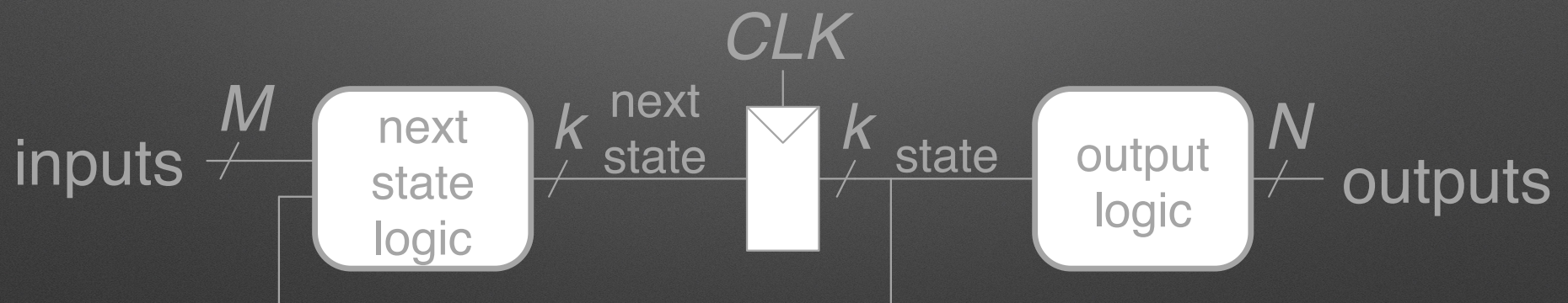

# Questions

- [State Machine Encoding Choices?]  
Memory vs. Logic: They can impact complexity of combinational logic.  
(Typically One-hot: more memory, but simpler logic))
- [FSMs? Mealy? Moore?]: More (Moore?) next time
- [I don't get/understand Latches/Edges/Levels/Flip-Flops/etc.]
- [Which memory things are important]: (Rising) Edge Triggered D-latch.  
(Most others were just part of the journey to it)

# Questions

- [What about async stuff / parallel? Does it matter? Where is it used?]
  - Yes, matters. Is often critical in high performance systems (real time computations, handling volumes of streaming data, etc.)
- Will we make FSMs? Yep.
- Are FSMs part of modern computers? Yes —they often handle the control of CPU operations. We'll see this later.
- Is this “clock” related to the computer clock? How does it relate to computer performance? It's the same basic idea. Much of a computer is controlled by a synchronous machine. The clock speed is based on propagation delay and dictates the speed of computations.

# Next Time

- Studio